

### Circuit Designs Using Analog Devices Products

Apply these product pairings quickly and with confidence. For more information and/or support call 1-800-AnalogD (1-800-262-5643) or visit [www.analog.com/circuit](http://www.analog.com/circuit).

Devices Connected/Referenced	
<a href="#">AD5292</a>	Digital Potentiometer, 10 bits, 1% Resistor Tolerance
<a href="#">AD8676</a>	Ultraprecision, Dual, Rail-to-Rail Output Op Amp
<a href="#">AD8541</a>	General-Purpose CMOS, Single, Rail-to-Rail Amplifier
<a href="#">ADCMP371</a>	Comparator with Push-Pull Output Stage

## Logarithmic Audio Volume Control with Glitch Reduction Using the AD5292 Digital Potentiometer

### CIRCUIT FUNCTION AND BENEFITS

This circuit provides a logarithmic audio volume control with glitch reduction using the AD5292 digital potentiometer in conjunction with the dual AD8676 and single AD8541 op amps, ADCMP371 comparators, and 7408 AND gates.

This circuit provides low total harmonic distortion (THD), a maximum signal attenuation of 46 dB, and a shutdown function that attenuates up to 130 dB, as shown in Figure 3. The AD5292 can be placed in shutdown mode by executing a software shutdown command. This feature places the RDAC in a special state in which terminal A is open-circuited and wiper W is connected to terminal B.

This circuit offers a logarithmic gain control function over an output voltage range of  $\pm 14$  V (10 V rms) and is capable of delivering up to  $\pm 20$  mA output current. The AD5292 is programmable over an SPI-compatible serial interface.

In addition, the AD5292 has an internal 20-times programmable memory that allows a customized volume setting at power-up.

This circuit provides low noise, low THD, high signal attenuation, low tempco, and high voltage capability. It is well suited for many audio applications.

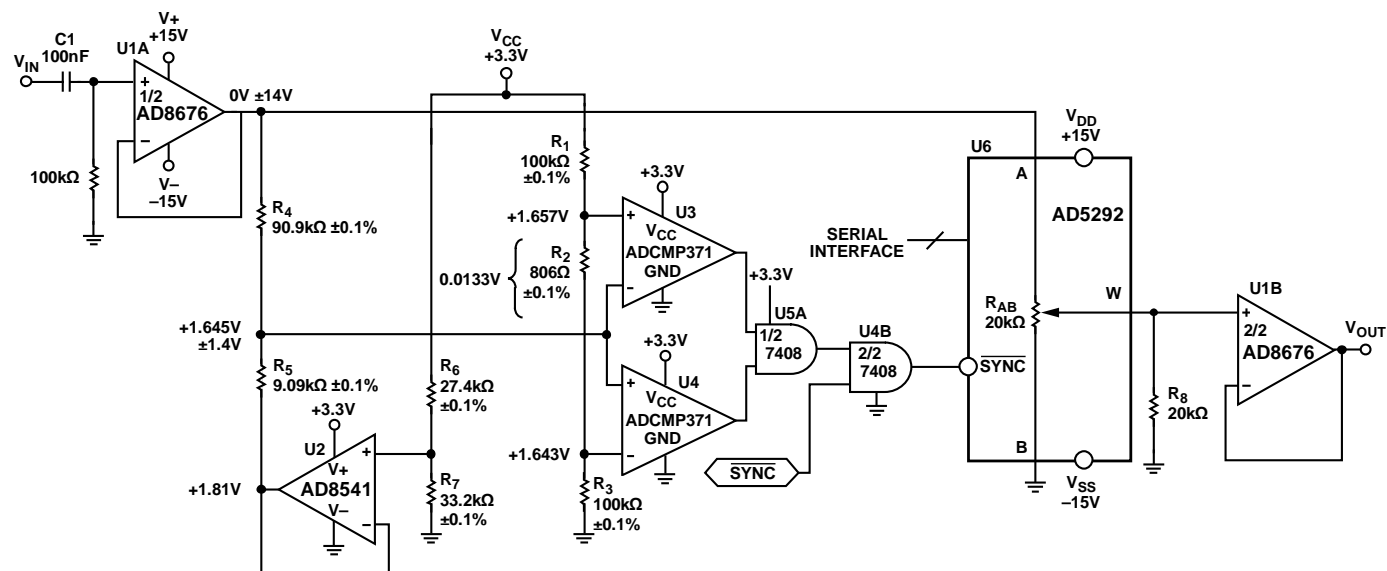


Figure 1. Logarithmic Audio Volume Control with Glitch Reduction (Simplified Schematic; Decoupling and All Connections Not Shown)

### Rev.A

"Circuits from the Lab" from Analog Devices have been designed and built by Analog Devices engineers. Standard engineering practices have been employed in the design and construction of each circuit, and their function and performance have been tested and verified in a lab environment at room temperature. However, you are solely responsible for testing the circuit and determining its suitability and applicability for your use and application. Accordingly, in no event shall Analog Devices be liable for direct, indirect, special, incidental, consequential or punitive damages due to any cause whatsoever connected to the use of any "Circuit from the Lab". (Continued on last page)

## CIRCUIT DESCRIPTION

This circuit employs the AD5292 digital potentiometer in conjunction with the dual AD8676 and single AD8541 op amps, ADCMP371 comparators, and 7408 AND gates, providing a low distortion logarithmic audio volume control with glitch reduction. The logarithmic taper is achieved by adding resistor R8 between the wiper connection and ground. This method is described in detail in the article “Tack a Log Taper onto a Digital Potentiometer” by Hank Zumbahlen, *EDN*, 1/20/00.

The circuit provides an input/output buffer, minimizing the load effects with other external circuits; the AD8676 dual op amp ensures low noise and precision rail-to-rail output voltage. Figure 2 shows the logarithmic output voltage,  $V_{OUT}$ , normalized by  $V_{IN}$ .

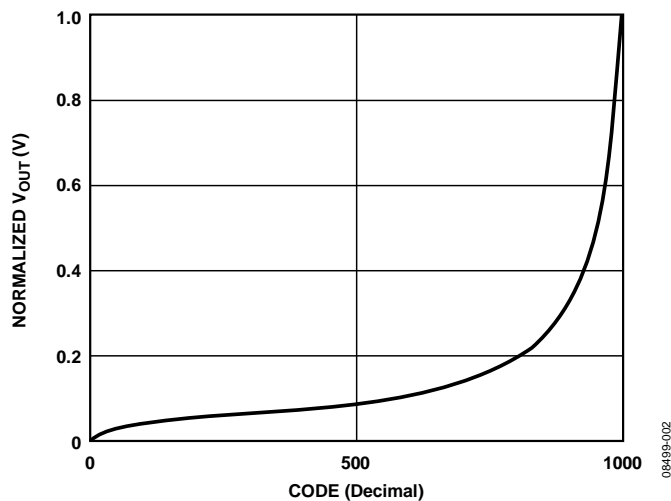


Figure 2. Normalized  $V_{OUT}$  vs. Code

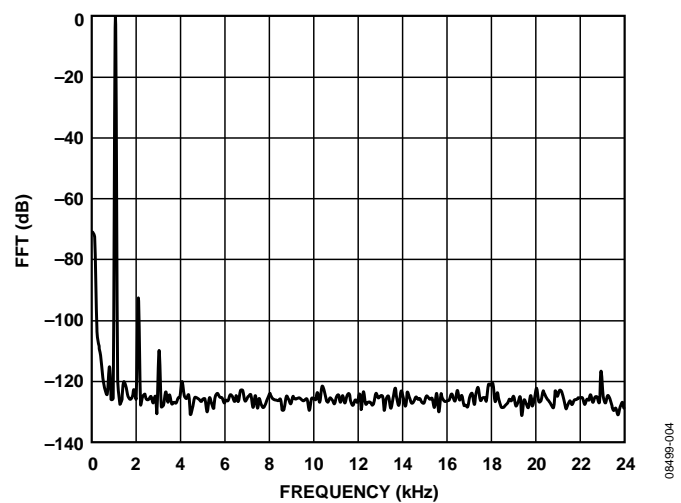


Figure 4. FFT for 1 kHz, 1  $V_{RMS}$  Input Signal, 0 dB Gain

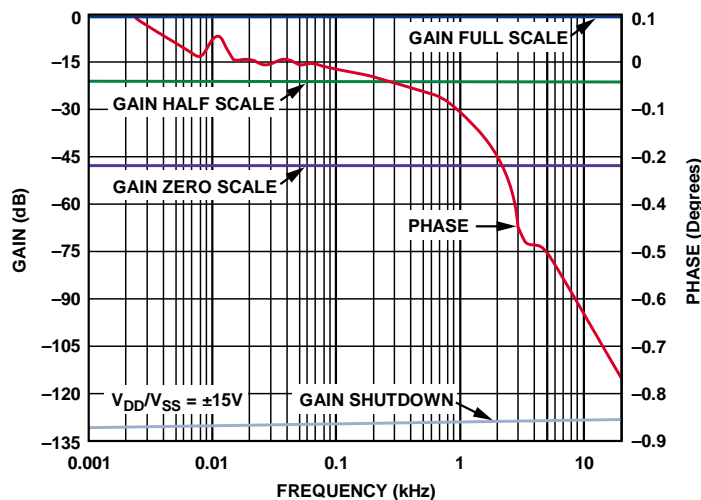


Figure 3. Gain and Phase vs. Frequency for 1  $V_{RMS}$  Input Signal

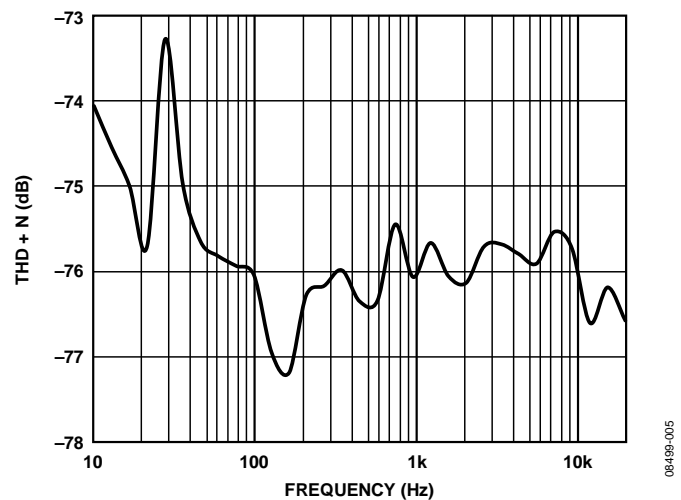


Figure 5. THD + Noise vs. Frequency, 1  $V_{RMS}$  Input Signal, 0 dB Gain

The glitch reduction circuit employs the AD8541, ADCMP371, and 7408 AND gates. Comparators U2 and U3 act as window comparators, with a 13.3 mV threshold between the two. This is large enough to overcome the typical comparator offset voltage. This circuit is a zero crossing detector that minimizes the glitch by allowing the attenuation to change only when the signal is crossing 0 V. Resistors R4 and R5 attenuate the input signal by 90.91% and establish the common-mode voltage of 1.645 V into the window comparator. The maximum uncertainty of the zero crossing is approximately 133 mV reflected to the input. The output of the window comparator is AND'd with the external  $\overline{\text{SYNC}}$  command to drive the  $\overline{\text{SYNC}}$  input of the AD5292. After the negative-going edge of  $\overline{\text{SYNC}}$  to the AD5292, the next clock pulse updates the internal DAC register.

Resistors R1 to R7 should be 0.1% tolerance to ensure an optimal zero cross detection, which provides a smaller energy glitch and prevents large attenuation step. The threshold window is approximately 133 mV referenced to the input signal voltage,  $V_{\text{IN}}$ . A typical attenuation step with glitch reduction circuit active is shown in Figure 9.

The AD5292 has 20-times programmable memory, which enables the user to preset the attenuation to a specific value at power-up.

Optimum layout, grounding, and decoupling techniques must be utilized in order to achieve the desired performance (see [Tutorial MT-031](#) and [Tutorial MT-101](#)). As a minimum, a 4-layer PCB should be used with one ground plane layer, one power plane layer, and two signal layers.

### COMMON VARIATIONS

The [AD5291](#) (8 bits with 20-times programmable power-up memory) and [AD5293](#) (10 bits, no power-up memory) are both  $\pm 1\%$  tolerance digital potentiometers that are suitable for this application.

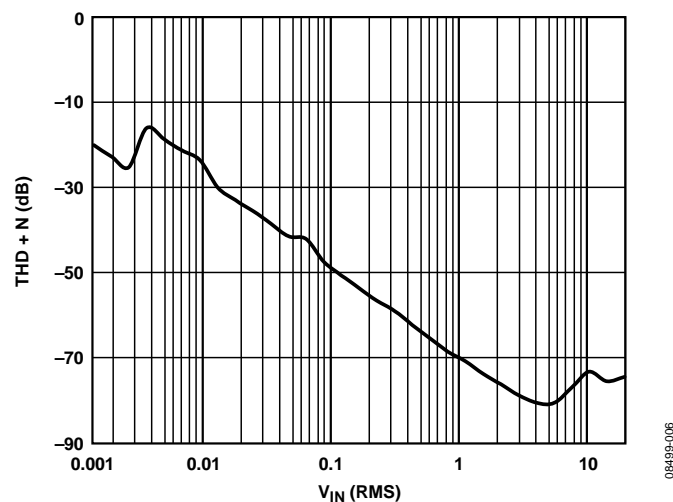


Figure 6. THD + Noise vs. 1 kHz Input Signal Amplitude, 0 dB Gain

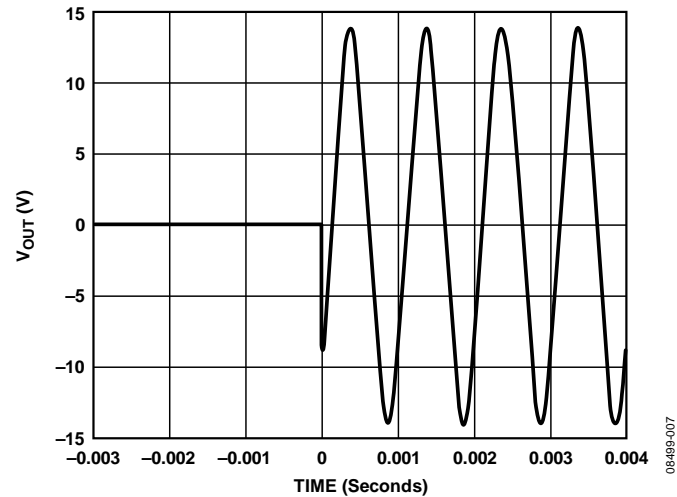


Figure 7. Large Step Change in Attenuation Shows Glitch Without Glitch Reduction Circuit

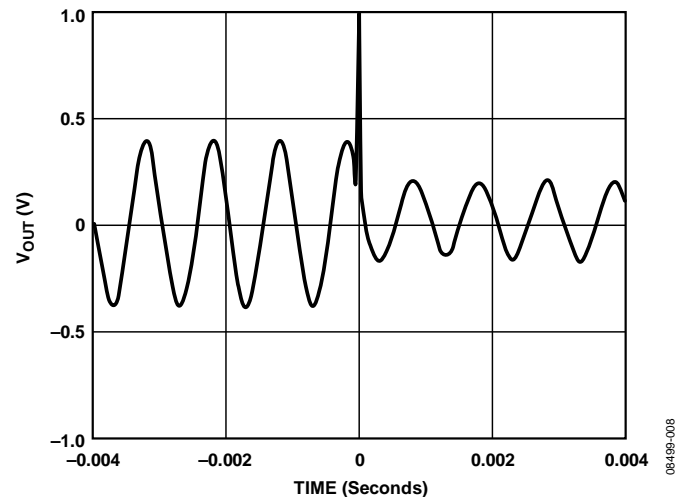


Figure 8. Small Change in Attenuation Showing Glitch Without Glitch Reduction Circuit

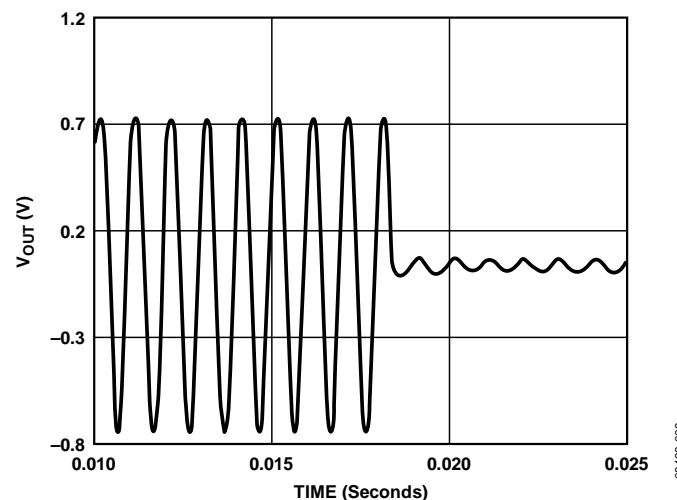


Figure 9. Glitch Reduction Circuit Activated

**LEARN MORE**

Zumbahlen, Hank. "Tack a Log Taper onto a Digital Potentiometer," *EDN*, January 20, 2000.

MT-031 Tutorial, *Grounding Data Converters and Solving the Mystery of "AGND" and "DGND"*. Analog Devices.

MT-087 Tutorial, *Voltage References*. Analog Devices.

MT-091 Tutorial, *Digital Potentiometers*. Analog Devices.

MT-101 Tutorial, *Decoupling Techniques*. Analog Devices.

**Data Sheets**

AD5292 Data Sheet

AD5291 Data Sheet

AD5293 Data Sheet

AD8676 Data Sheet

AD8541 Data Sheet

ADCMP371 Data Sheet

**REVISION HISTORY****3/10—Rev. 0 to Rev. A**

Changes to Circuit Function and Benefits Section ..... 1

**10/09—Revision 0: Initial Version**

(Continued from first page) "Circuits from the Lab" are intended only for use with Analog Devices products and are the intellectual property of Analog Devices or its licensors. While you may use the "Circuits from the Lab" in the design of your product, no other license is granted by implication or otherwise under any patents or other intellectual property by application or use of the "Circuits from the Lab". Information furnished by Analog Devices is believed to be accurate and reliable. However, "Circuits from the Lab" are supplied "as is" and without warranties of any kind, express, implied, or statutory including, but not limited to, any implied warranty of merchantability, noninfringement or fitness for a particular purpose and no responsibility is assumed by Analog Devices for their use, nor for any infringements of patents or other rights of third parties that may result from their use. Analog Devices reserves the right to change any "Circuits from the Lab" at any time without notice, but is under no obligation to do so. Trademarks and registered trademarks are the property of their respective owners.